

Logic Gates Reference Guide

- AND: Output is HIGH if all inputs are HIGH
- OR: Output is HIGH if any input is HIGH
- NOT: Inverts the input
- NAND: Opposite of AND
- NOR: Opposite of OR
- XOR: Output is HIGH if inputs are different
- XNOR: Output is HIGH if inputs are the same